			170 200 17		
X <sub>1</sub> X <sub>2</sub>	00	01	11	10	
0	1	1	0	0	
1	1	0	0	1	

	7	X, X <sub>2</sub>			
1	4			11	10
/ <b>=</b> 1	0	M	1	0	0
	,				

5	= ,	X

## LA RICORDARE

$y \rightarrow y'$	J	K	
$0 \rightarrow 0$	0	-	
$0 \rightarrow 1$	1	-	
$1 \rightarrow 0$	-	1	
$1 \rightarrow 1$	-	0	

,	о <i>э</i>	01	11	10				
0	_	_			}	<b>=</b>	- /	, 2
1	0	1	1	$\bigcirc$				

X1X2	00	01	11	10	d_
0	0	0	1	1	R=
1	0	0	1	1	

$y \rightarrow y'$	S	R
$0 \rightarrow 0$	0	-
$0 \rightarrow 1$	1	0
$1 \rightarrow 0$	0	1
$1 \rightarrow 1$	-	0